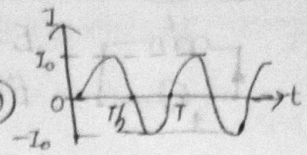


Alternating Current

$E = E_0 \sin \omega t$, $E_0 \cos \omega t$
 $I = I_0 \sin \omega t$, $I_0 \cos \omega t$
 $P = E_{rms} I_{rms}$

$E_0 \sin(\omega t + \phi)$, $E_0 \cos(\omega t + \phi)$
 $I_0 \sin(\omega t + \phi)$, $I_0 \cos(\omega t + \phi)$




Average voltage $V_{avg} = E_{avg} = \frac{\int_{t_1}^{t_2} E_{inst} dt}{\int_{t_1}^{t_2} dt} = \frac{\int_0^T E_0 \sin \omega t dt}{\int_0^T dt}$

i) for complete cycle $t_1 = 0, t_2 = T = 2\pi/\omega$
 $V_{avg} = 0$

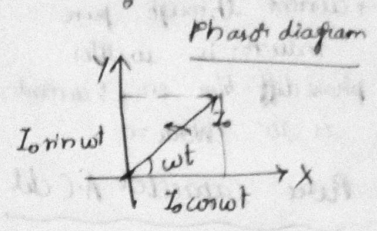ii) for half cycle $t_1 = 0, t_2 = T/2 = \pi/\omega$

$V_{avg} = \frac{\int_0^{T/2} E_{inst} dt}{\int_0^{T/2} dt} = \frac{2V_0}{\pi} = 0.63 V_0$



average current i) for complete cycle $\langle I \rangle = I_{avg} = \frac{\int_0^T I_0 \sin \omega t dt}{\int_0^T dt} = 0$

ii) for half cycle $\langle I \rangle = \frac{2I_0}{\pi} = 0.63 I_0$

RMS voltage $V_{rms}^2 = \frac{\int_0^T V_{inst}^2 dt}{\int_0^T dt} = \frac{V_0^2}{2} \Rightarrow V_{rms} = \frac{V_0}{\sqrt{2}} = 0.707 V_0$

$I_{rms}^2 = \frac{\int_0^T I^2 dt}{\int_0^T dt}$ $I_{rms} = \frac{I_0}{\sqrt{2}} = 0.707 I_0$ (ammeter reads only I_{rms})

average power $\langle P \rangle = E_{rms} I_{rms} \cos \phi = \text{true power}$

$= \frac{E_0 I_0}{2} \cos \phi$


$P_{app} = E_{rms} I_{rms} = \frac{E_0 I_0}{2}$

Power factor $= \cos \phi = \frac{P_{true}}{P_{app}} = \frac{V_R}{V} = \frac{V}{V} = \frac{V_L}{V} = \frac{R}{Z}$

form factor $= \frac{I_{rms}}{I_{avg}} = \frac{V_{rms}}{V_{avg}} = \frac{\pi}{2\sqrt{2}} = 1.11$


peak factor $= \frac{V_0}{V_{rms}} = \frac{I_0}{I_{rms}} = \frac{V_0}{V_0/\sqrt{2}} = \sqrt{2}$

Power resistor AC circuit

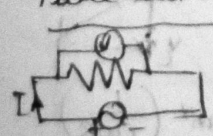


$V_R = E = E_0 \sin \omega t$
 $IR = E_0 \sin \omega t \Rightarrow I = I_0 \sin \omega t$

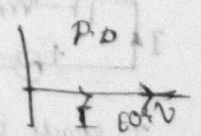power factor, $\cos \phi = 1$
 $\phi = \phi_2 - \phi_1 = 0$
 $\langle P \rangle = \frac{E_0 I_0}{2}$



Pure inductor A.C.ckt

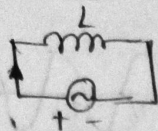

$$E = E_0 \sin \omega t$$

$$E = L \frac{di}{dt} = I(Z), \quad I = I_0 \sin(\omega t - \pi/2)$$

$$\Delta \phi = \phi_V - \phi_I = -\pi/2 \quad (\pi/2 \text{ lagging})$$

Power factor, $\cos \phi = 0$, $\langle P \rangle = 0$

* induced emf = applied emf

→ current through pure inductor is wattless.
phase diff. b/w emf & current is 90° . Work = 0

$$I_0 = \frac{E_0}{L\omega}$$


$$X_L = Z = L\omega$$

$$\sin \phi = \frac{\omega L}{Z}$$

X_L - reactance offered by inductor

at high

Pure capacitor A.C.ckt

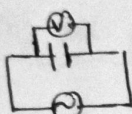


$$E = E_0 \sin \omega t$$

$$\phi_V < \phi_I \Rightarrow I = I_0 \sin(\omega t + \pi/2)$$

$$\phi = \phi_V - \phi_I = \pi/2 \quad (\text{leading})$$


X_C - reactance offered by capacitor

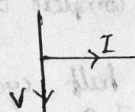

$$\langle P \rangle = 0$$

$$Z = X_C = 1/\omega C$$

L-R ckt

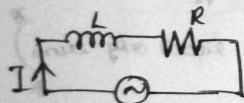


$$E = E_0 \sin \omega t$$

$$V_L = IR$$

$$E - V_L = V_R \Rightarrow E - L \frac{di}{dt} = IR$$

$$I = I_0 \sin(\omega t - \phi)$$

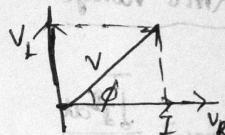

$$\rightarrow V = \sqrt{V_R^2 + V_L^2}, \quad Z = \sqrt{R^2 + L^2 \omega^2}$$


→ I lags E by ϕ

$$\tan \phi = \frac{V_L}{V_R} \Rightarrow \phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) \Rightarrow \tan^{-1} \left(\frac{IX_L}{IR} \right) = \tan^{-1} \left(\frac{L\omega}{R} \right)$$

$$\text{power factor, } \cos \phi = \frac{V_R}{V} = \frac{V_R}{\sqrt{V_R^2 + V_L^2}}$$

$$\langle P \rangle = E_{\text{rms}} I_{\text{rms}} \cos \phi = \frac{E_0 I_0}{2} \left(\frac{R}{\sqrt{R^2 + L^2 \omega^2}} \right)$$


C-R ckt

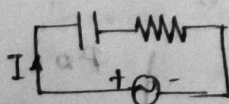

$$E = E_0 \sin \omega t$$


$$E - V_C = IR \Rightarrow E - q/C = IR$$
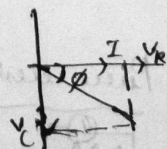
$$\tan \phi = \frac{V_C}{V_R} = \frac{1}{\omega R C} \Rightarrow \phi = \tan^{-1} \left(\frac{1}{\omega R C} \right)$$



→ I leads E by ϕ

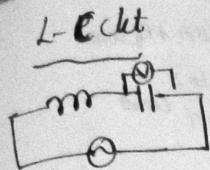
$$\text{power factor } \cos \phi = \frac{V_R}{V} = \frac{V_R}{\sqrt{V_R^2 + V_C^2}}$$



$$E = E_0 \sin \omega t$$

$$E = V_L + V_C \Rightarrow I = I_0 \sin(\omega t - \pi/2) \text{ if } (V_L > V_C)$$
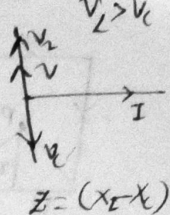
$$I = I_0 \sin(\omega t + \pi/2) \text{ if } (V_L < V_C)$$




$X_L > X_C$ lags

$X_L < X_C$ I leads

$$\phi = +\pi/2 \text{ (if } V_L < V_C \text{ or } X_L < X_C)$$
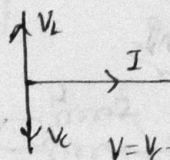
$$= -\pi/2 \text{ (if } V_L > V_C \text{ or } X_L > X_C)$$



$$V = V_C - V_L$$

$$V = I(X_C - X_L)$$

at high frequency
 $\omega L \gg 1/\omega C$
 at low frequency
 $1/\omega C \gg \omega L$
 LCR series ckt:

power factor = $\cos \phi = 0$

$$\langle P \rangle = E_{\text{rms}} I_{\text{rms}} \cos \phi = 0$$


$$E = E_0 \sin \omega t$$

$$E - V_L - V_C = IR$$

$$I = I_0 \sin(\omega t + \phi) \text{ if } V_L < V_C$$

$$X_L < X_C$$
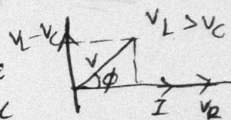
$$I = I_0 \sin(\omega t - \phi) \text{ if } V_L > V_C \text{ or } X_L > X_C$$



$$V = \sqrt{V_R^2 + (V_L - V_C)^2}, \quad Z = \sqrt{R^2 + (\omega L)^2 + (1/\omega C)^2 - 2L/C}$$

$$\text{power factor} = \cos \phi = \frac{R}{(\omega L - 1/\omega C)}$$

$$\phi = \tan^{-1} \left(\frac{\omega L - 1/\omega C}{R} \right)$$

$$P_{\text{avg}} = E_{\text{rms}} I_{\text{rms}} \cos \phi = \frac{E_0 I_0}{2} \left(\frac{R}{X_L - X_C} \right) \neq 0$$

LCR resonance:

applied = δ ckt then ckt is at resonance

$$I \rightarrow I_{\text{max}}$$

$$Z \rightarrow Z_{\text{min}}$$

at resonance

$$X_C = X_L$$

Power $> V_{\text{rms}} I_{\text{rms}}$

$$Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$


$$Z_{\text{LCR}} = R$$

$$\omega^2 = 1/LC, \quad \omega = 1/\sqrt{LC} = \omega_r$$

$$\phi_r = \frac{1}{2\pi \sqrt{LC}}$$

it is independent on resistor X_L
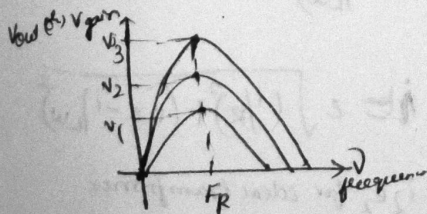
$$V_{\text{gain}} = \frac{V_{\text{out}}}{V_{\text{in}}}, \quad I_{\text{gain}} = \frac{I_{\text{out}}}{I_{\text{in}}}$$



$$V_3 > V_2 > V_1 \Leftrightarrow R_3 < R_2 < R_1$$


$$\text{Quality factor or Q-factor}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{F_r}{\text{Bandwidth } (F_H - F_L)}$$

$$\Delta \omega = \omega_2 - \omega_1 = R/L$$


$$Q = \frac{\omega_r}{\Delta \omega}$$

11el RLC ckt

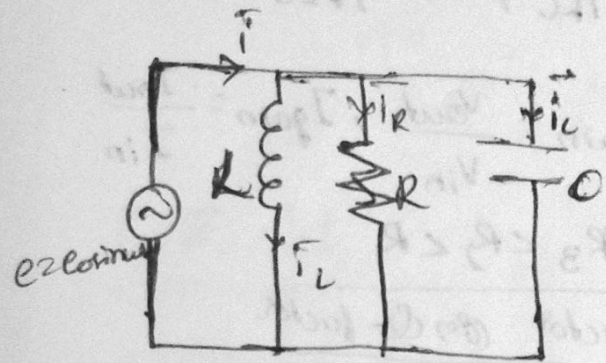

$$i = \bar{i}_R + \bar{i}_L + \bar{i}_C = \sqrt{i_R^2 + (i_L - i_C)^2}$$
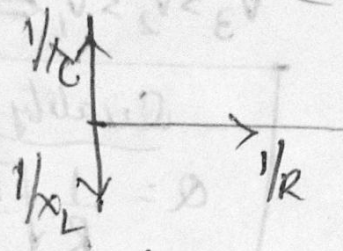
$$1/Z = \sqrt{(1/R)^2 + (\omega C - 1/L\omega)^2}$$



$$i = e \sqrt{(1/R)^2 + (\omega C - 1/L\omega)^2}$$

$$\omega_R = 1/\sqrt{LC}$$

, $i_1 e_1 = i_2 e_2$ for ideal transformer

$$\eta = \frac{V_s i_s}{i_p V_p} \times 100\% = \frac{V_p i_p - P_{loss}}{V_p i_p} \times 100\%$$